




EEE 303 – Digital Electronics

Lecture-7 – Verilog for Logic Synthesis

Dr. Sajid Muhaimin Choudhury
Dept of EEE, BUET

1

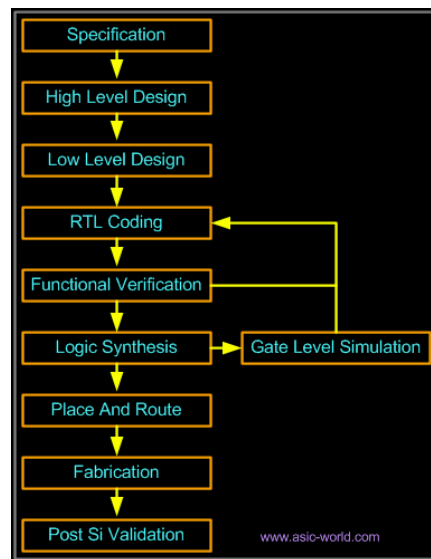


3/9/20

2

2

High Level Design

 


3/9/20

3

3

Low Level Design

 

3/9/20

4

4

RTL Coding

- Register Transfer Logic
- Micro design is converted into Verilog/VHDL code, using synthesizable constructs of the language.

3/9/20

5

5

Verilog Module

- An elementary Verilog program is called a *module*.
- A module corresponds to a digital circuit. Modules have input and output *ports* that correspond to the input
- and output terminals of a digital circuit.
- The ports and variables used to represent internal signals are declared at the beginning of the program.
- Modules have other statements used to define how it transforms the input signals to output signals.

3/5/20

6

6

Structural vs Behavior

- **Structural modules** consist of a list of component modules (defined elsewhere) and a list of wires used to interconnect the modules.
- **Behavior modules** specify the output signals as functions of the input signals. They need not give any indication of the structure of the circuit.


3/5/20

7

7

Example of a behavioral Verilog module

- Circuit:

 

- Verilog module:

```
module circuit1b (A, B, C, D, E, X, Y, Z);
input A, B, C, D, E;
output X, Y, Z;
assign X = ~((A ^ B) | C);
assign Y = ~((B & C) | D) & E;
assign Z = A | D | (B & C);
endmodule
```

3/5/20

8

8

Verilog Input and Output

- Individual signals (e.g., A, B, ... in the previous example) can take any of the following four values:
 - 0 = logic value 0
 - 1 = logic value 1
 - z = tri-state (high impedance) x = unknown value
- The unknown value is used by simulators to indicate that they do not know how to determine a signals value (e.g., the user has not specified a value for an input signal). The tri-state value means that no signal is assigned to the variable.
- The unknown value x can also be used to specify a don't care condition to the synthesis tools.
- Note that ports must be listed in the module statement (first line) and their direction (input or output) declared in the following statements.

3/5/20

9

9

- The three **assign** statements are independent and can execute in any order or concurrently.
- The right side of an **assign** statement is evaluated and its resulting value assigned to the signal on the left side whenever one of the signals used in the right side changes value.
- This type of assignment is also called a *continuous assignment*.
- This method of interpreting the execution of **assign** statements is quite different
- from that use in conventional programming languages in the following ways:
 - Two or more assignments can execute simultaneously. This is necessary to represent the timing characteristics of hardware systems.
 - An assignment executes whenever it is ready (i.e., has new data for the variables on its right side)
 - There is no concept of "locus of control" or "program counter" that determines the next instruction to execute. Therefore, the order the assignments are written does not matter
 - This method of assignment statement execution is sometimes called *non-procedural or data-driven* execution, where conventional programming languages are said to be *procedural*.

3/5/20

10

10

Behavioral vs. Structural Verilog Descriptions

- The previous example is a behavioral descriptions because it specifies the logical values of the circuit's outputs as logical equations with no reference to how the gates in a possible implementation might be interconnected.
- It is also possible to specify a structural description in Verilog that specifies explicitly how a set of smaller components (e.g., gates) are interconnected to form a larger system as shown on the following slide.
- Note that the internal connections from gate outputs to gate inputs are declared to be of type **wire**.
- These wire declarations could be omitted as long as the component modules are simple gates. Verilog will assume that any gate output signal that is not declared is of type **wire**.
- Each gate is specified by its name (e.g., **and**, **or**, ...) and a list of ports or wires connected to its terminals. All gates have a single output and it is always listed first in this list.


3/5/20

11

11

Structural Verilog
 
```
module circuit1s (A, B, C, D, E, X, Y, Z);  
input A, B, C, D, E;  
output X, Y, Z;  
wire T1, T2, T3, T4, T5, T6, T7;  
xor(T1, A, B);  
or(T2, T1, C);  
not(X, T2);  
and(T3, B, C);  
or(T4, T3, D);  
not(T5, T4);  
and(Y, T5, E);  
or(T6, A, D);  
and(T7, B, C);  
or(Z, T6, T7);  
endmodule
```



3/5/20

12

12

Procedural Block (Always Blocks)

- A procedural block is a construct that contains statements that are executed procedurally (i.e., in the order they are written).
always *@(sensitivity_list)*
 begin
 procedural statements
 end
- The sensitivity list is a list of signals separated by **or**.
 - When any one of the signals in the sensitivity list changes value, the always block wakes up, executes its procedural statements, and then goes back to sleep.
- The always block acts like a generalized assign statement where the action that takes place can be specified by sequential code.

3/5/20

13

13

Always Block Example

```
module always_example(x, y, z);  
    input x, y;  
    output z;  
    reg z, s;  
    always @(x or y)  
    begin  
        s = x ^ y;  
        z = x & s;  
    end  
endmodule
```

3/5/20

14

14

Reg variable

- Variables declared as type **reg** hold their value until they are assigned a new value. It is said that the assigned value is *registered* in the variable
- Whenever x or y changes value, the always block is executed as follows:
 - First, the statement $s = x \wedge y$ executes and registers a new value in s
 - Next, the statement $z = x \& s$ executes using the new value of s that it received when the first statement was executed.
 - Then the block stops executing and waits for either x or y to change again.
- Variables on the left side of a procedural statement must be declared as type **reg**.
- The main advantage of using always blocks to represent combinational circuits is that you can use control statements such as “if then else” as illustrated by the following example

3/5/20

15

15

Explain how the behaviors of the following two modules differ

<pre>module always_example(x, y, z, f); input x, y, z; output f; reg f, s; always @(x or y or z) begin s = x ^ y; f = z & s; end endmodule</pre>	<pre>module assign_example (x, y, z, f); input x, y, z; output f; wire s; assign s = x ^ y; assign f = z & s; endmodule</pre>
--	--

3/5/20

16

16

Conditions for combinational behavior of always blocks

- The following conditions are necessary for an always block to represent combinational logic (as opposed to sequential logic)
 - All reg, wire and input signals that appear on the right side of an assignment statement within the always block must appear in the sensitivity list
 - We call a sensitivity list that satisfies this condition a *complete sensitivity list*.
 - All signals in the sensitivity list must appear without edge specifiers
 - Edge specifiers indicate that a signal is asserted by a change in value as opposed to its level (e.g., a rising edge or falling edge). They are introduced and utilized in later chapters on sequential circuits.
- All output signals must be assigned a value every time the always block executes
- These conditions guarantee that the input signals uniquely determine the output signals, which is the very definition of a combinational circuit.
- A sensitivity list of the form @(*) is shorthand for a complete list. It is recommended that you use this notation for combinational always block

17

17

Example (Incomplete sensitivity list)

```
module example1(a, b, c, f);  
input a, b, c;  
output f;  
reg f;  
always @(a, b)  
    if (a==1)  
        f = b;  
    else  
        f = c;
```

3/5/20

18

18

Logic Operation

Operator Type	Operator Symbol	Operation Performed
Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	+	Unary plus
	-	Unary minus
Logical	!	Logical negation
	&&	Logical and
		Logical or
Relational	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal
Equality	==	Equality
	!=	inequality
Reduction	~	Bitwise negation
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
Shift	>>	Right shift
	<<	Left shift
Concatenation	{ }	Concatenation
Conditional	?	conditional

3/9/20

19

19

Examples

- $a = b + c ;$
- $a = 1 \ll 5 ;$
- $a = !b ;$
- $a = \sim b ;$

3/9/20

20

20

If-else-end

```
1 // begin and end act like curly braces in C/C++.
2 if (enable == 1'b1) begin
3     data = 10; // Decimal assigned
4     address = 16'hDEAD; // Hexadecimal
5     wr_enable = 1'b1; // Binary
6 end else begin
7     data = 32'b0;
8     wr_enable = 1'b0;
9     address = address + 1;
10 end
```

3/9/20

21

21

Case

```
1 case(address)
2     0 : $display ("It is 11:40PM");
3     1 : $display ("I am feeling sleepy");
4     2 : $display ("Let me skip this tutorial");
5     default : $display ("Need to complete");
6 endcase
```

It's a good idea to have a **default** case. If the Verilog machine enters into a non-covered statement, the machine hangs. Defaulting the statement with a return to idle keeps us safe.

3/9/20

22

22

While

A while statement executes the code within it repeatedly if the condition it is assigned to check returns true.

```
1 while (free_time) begin
2   $display ("Continue with webpage development");
3 end
```

3/9/20

23

23

While - counter

```
1 module counter (clk,rst,enable,count);
2 input clk, rst, enable;
3 output [3:0] count;
4 reg [3:0] count;
5
6 always @ (posedge clk or posedge rst)
7 if (rst) begin
8   count <= 0;
9 end else begin : COUNT
10  while (enable) begin
11    count <= count + 1;
12    disable COUNT;
13  end
14 end
15
16 endmodule
```

3/9/20

24

24

For

```
1  for (i = 0; i < 16; i = i + 1) begin
2      $display ("Current value of i is %d", i);
3  end
```

3/9/20

25

25

Initial Block

- An initial block, as the name suggests, is executed only once when simulation starts. This is useful in writing test benches.

```
1  initial begin
2      clk = 0;
3      reset = 0;
4      req_0 = 0;
5      req_1 = 0;
6  end
```

3/9/20

26

26



EEE 303 – Digital Electronics

Lecture-8 – Combinational Logic

Dr. Sajid Muhaimin Choudhury
Dept of EEE, BUET

27

EXAMPLE 5-1

In a certain chemical-processing plant, a liquid chemical is used in a manufacturing process. The chemical is stored in three different tanks. A level sensor in each tank produces a HIGH voltage when the level of chemical in the tank drops below a specified point.

Design a circuit that monitors the chemical level in each tank and indicates when the level in any two of the tanks drops below the specified point.


 


FIGURE 5-2

28

Inverted Logic: SOP vs POS

 

3/9/20

29

29

Universal Gates


- NAND
- NOR

3/5/20

30

30

NAND as Universal Gate

 

3/5/20

31

31

- Implement the following function with NAND logic only:
- $X = AB + CD$

3/5/20

32

32

$$X = AB + CD$$


$$\begin{aligned} X &= \overline{(\overline{AB})(\overline{CD})} \\ &= \overline{(\overline{A} + \overline{B})(\overline{C} + \overline{D})} \\ &= \overline{(\overline{A} + \overline{B})} + \overline{(\overline{C} + \overline{D})} \\ &= \overline{\overline{A}}\overline{\overline{B}} + \overline{\overline{C}}\overline{\overline{D}} \\ &= AB + CD \end{aligned}$$

3/5/20

33

33

NAND Implementation

 


(a) Original NAND logic diagram showing effective gate operation relative to the output expression

3/5/20

34

34

NAND to AND-OR logic

 


3/5/20

35

35

Dual Symbols

 

36


NAND with Dual Symbols

- All logic diagrams using NAND gates should be drawn with each gate represented by either a NAND symbol or the equivalent negative-OR symbol to reflect the operation of the gate within the logic circuit.
- The NAND symbol and the **negative-OR** symbol are called *dual symbols*.
- When drawing a NAND logic diagram, choose gate symbols in a way that every connection between a gate output and a gate input is either **bubble-to-bubble** or **nonbubble-to-nonbubble**.

3/5/20

37

37

 


(a) Several Boolean steps are required to arrive at final output expression.

3/5/20

38

38

Dual Symbol Representation

 

(b) Output expression can be obtained directly from the function of each gate symbol in the diagram.

3/5/20

39

39


NOR as Universal Gate



(a) One NOR gate used as an inverter



(b) Two NOR gates used as an OR gate

 


(c) Three NOR gates used as an AND gate

3/5/20

40

40

$$X = (A + B)(C + D)$$

 


3/5/20

41

41

NOR to AND-OR Logic

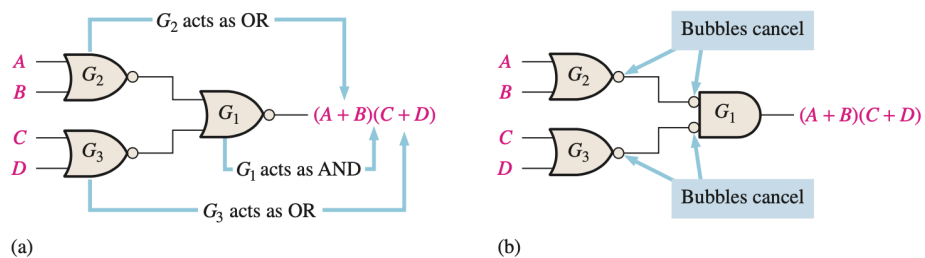

3/5/20

42

42

(a) Final output expression is obtained after several Boolean steps.

$$\begin{aligned} & \overline{\overline{A+B+C+D+E+F}} \\ &= \overline{(A+B+C+D)(E+F)} \\ &= \overline{(A+B+C+D)}(E+F) \\ &= ((A+B)\overline{C} + D)(E+F) \end{aligned}$$

3/5/20

43

43

(b) Output expression can be obtained directly from the function of each gate symbol in the diagram.

3/5/20

44

44